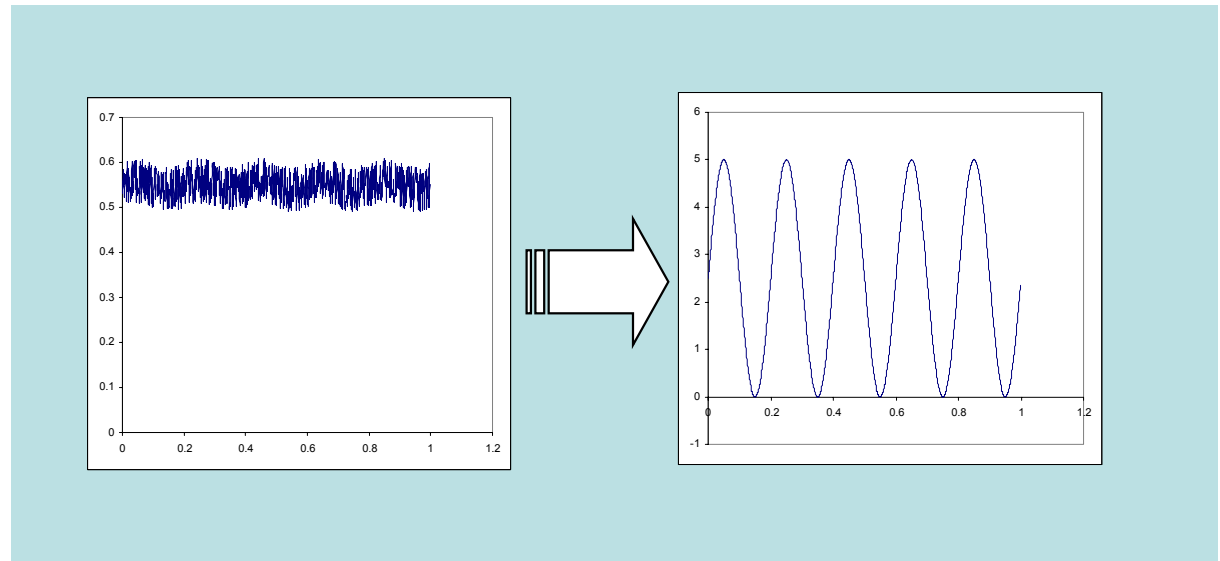


Using the Anadigm[®] FPAA to Interface With Sensors – Technical Considerations



Sensor Signal Conditioning Needs

- **Common signal conditioning tasks:**
 - Amplification
 - Offset removal
 - Rectification
 - Filtering



Sensor Signal Conditioning Needs

- Common conditioning tasks

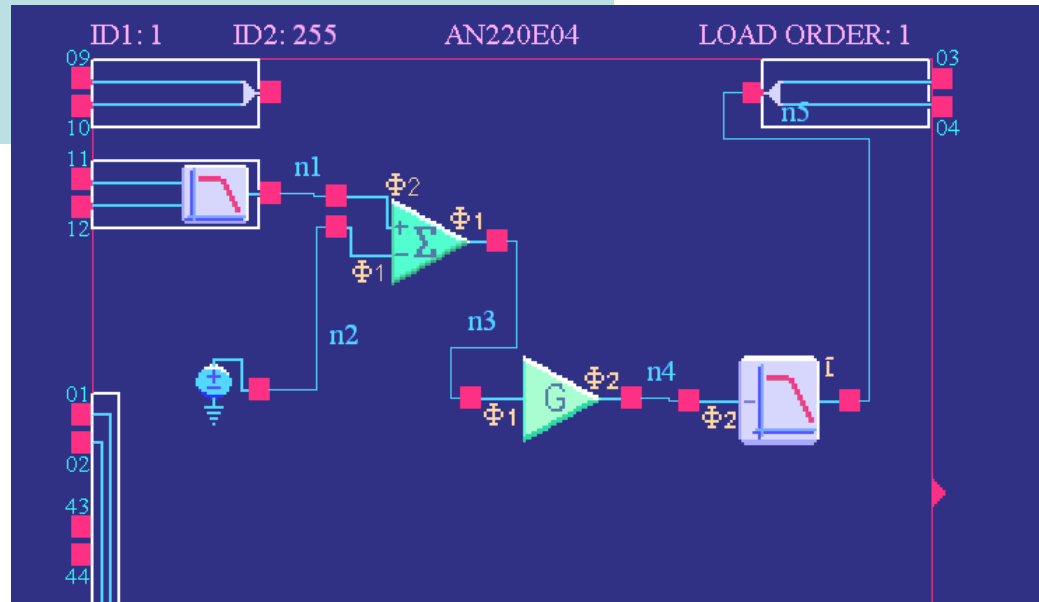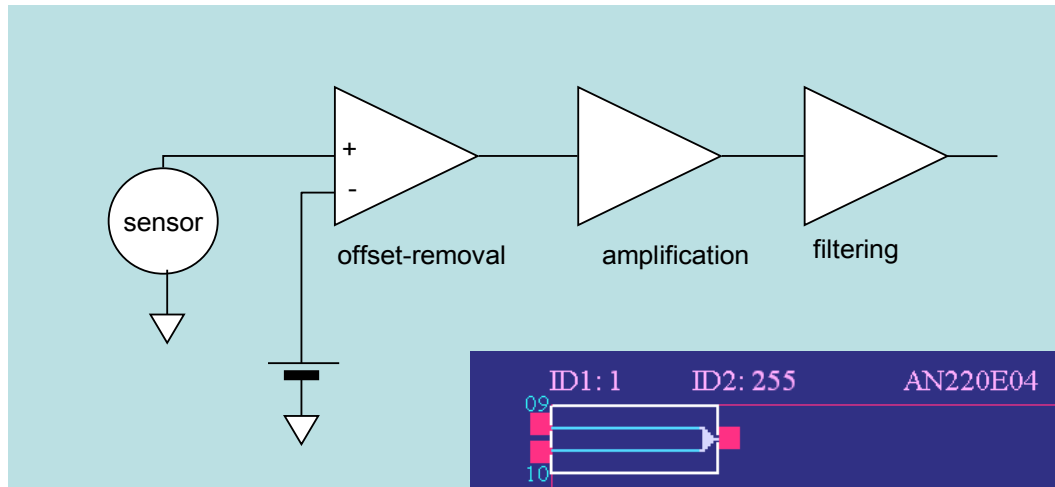


Operating Limits (1): High Clock Frequencies

- **Finite OpAmp bandwidth**

- Capacitors must charge or discharge within each half clock-cycle
- OpAmp speed affects settling-time

- **Non-zero switch resistance**

- Similar effect on settling-time

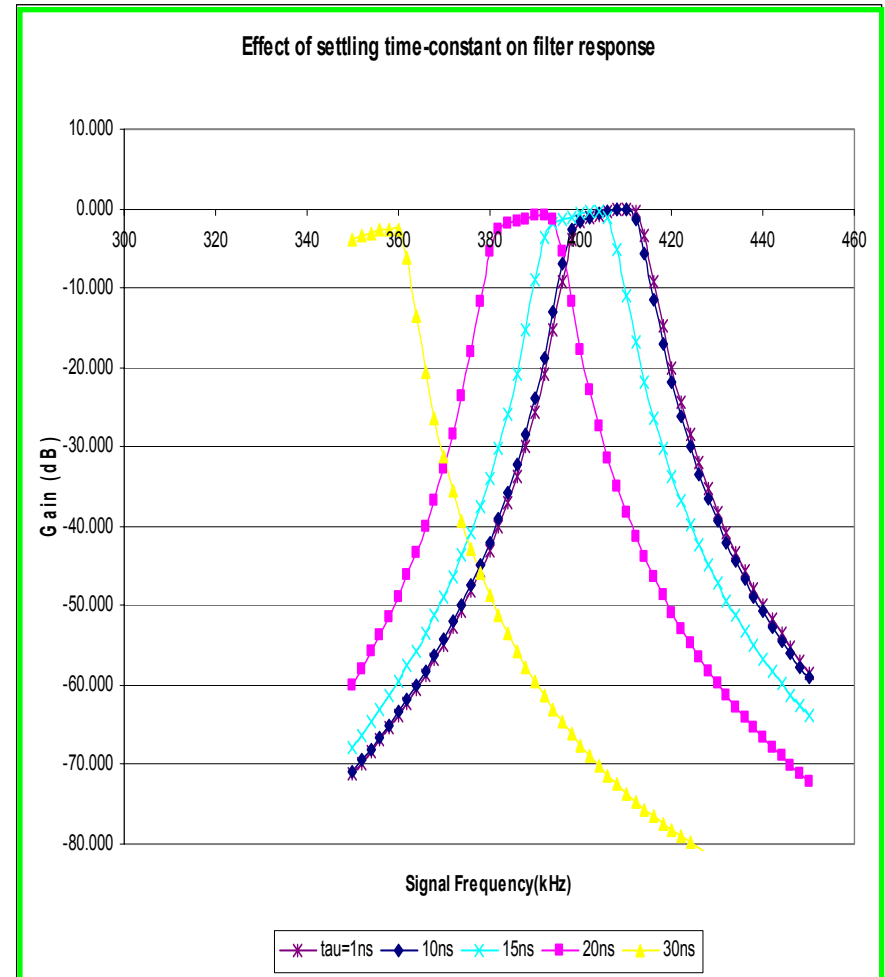

Operating Limits (2): High Signal Frequencies



- **Finite OpAmp Gain**

- Provided opamp has high *open-loop* gain and high input-resistance then:

$$\frac{1}{G} = -\frac{R1}{R2}$$

- If open-loop gain is not infinite then:
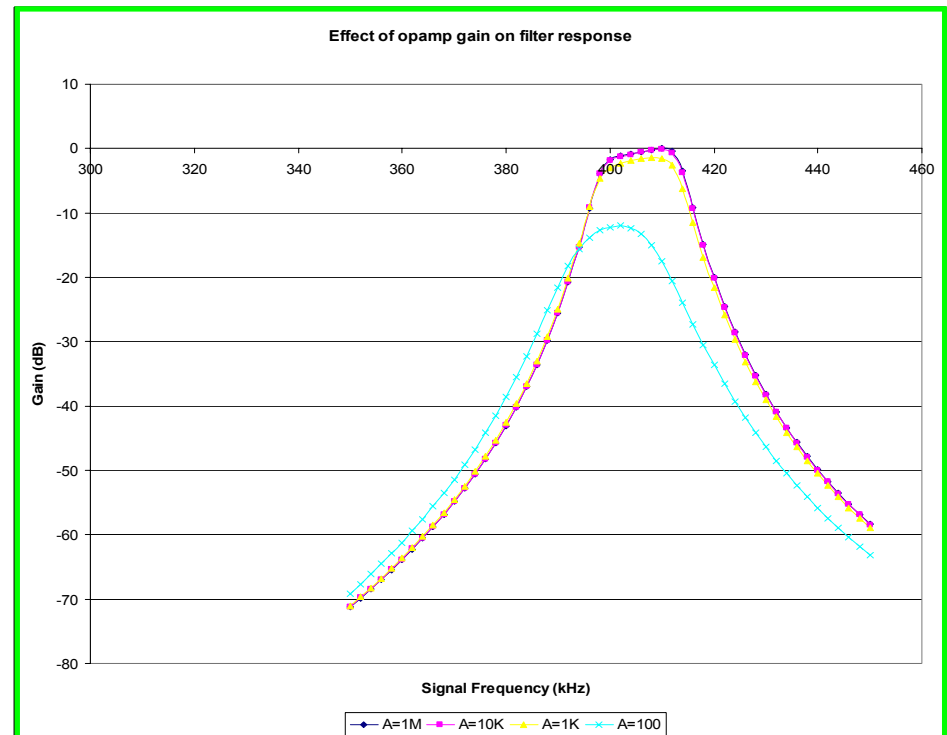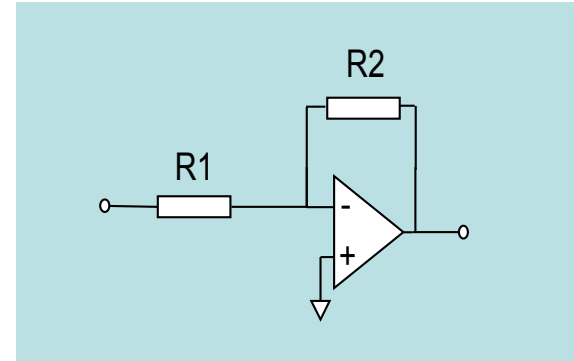
$$\frac{1}{G} = -\frac{R1}{R2} \left(1 + \frac{1}{A} \right) - \frac{1}{A}$$



Operating Limits (3): Low Clock Frequencies

- “Droop”

- The charge that should be stored on a node is:

$$Q = C.V$$

- This charge will be changed (+ or -) by leakage:

$$\Delta Q_L = I_L.T$$

- So, the error will be
Error = $I_L.T / C.V$

- For a specified max error:

$$T < \frac{(C.V)_{\min} \cdot \text{Error}}{(I_L)_{\max}}$$

So, using some approximate values:

- $C \cong 10^{-11}$ (farad)
- $V \cong 10^{-3}$ to 1 (volt)
- So, $CV \cong 10^{-11}$ to 10^{-14} (coulomb)
- $I_L \cong 10^{-15}$ to 10^{-18} (amperes)


For a leakage errors of 0.1% or less:

$$T < (C.V)_{\min} \cdot \text{Error} / (I_L)_{\max} \cong 10^{-14} \cdot 10^{-3} / 10^{-15} \cong 10^{-2} \text{ (secs)}$$


We can obtain leakage errors of 0.1% or less for millivolt signals, for sampling frequencies in the low kHz range.

- **Offset errors**

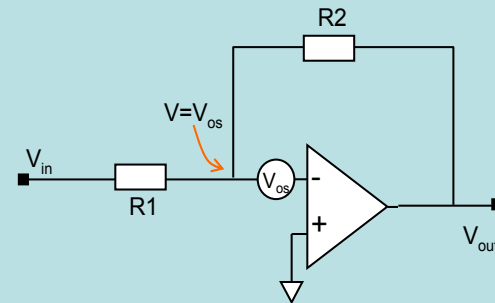- Slight mismatches inside the opamp require balancing with a small input voltage
- Output voltage will have a DC error



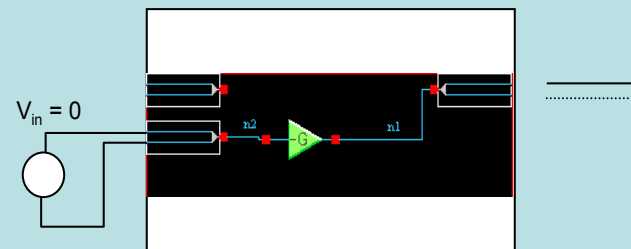
$$V_{out} = -V_{in} \cdot \frac{R2}{R1} + V_{os} \left(\frac{R2}{R1} + 1 \right)$$




Offset Compensation

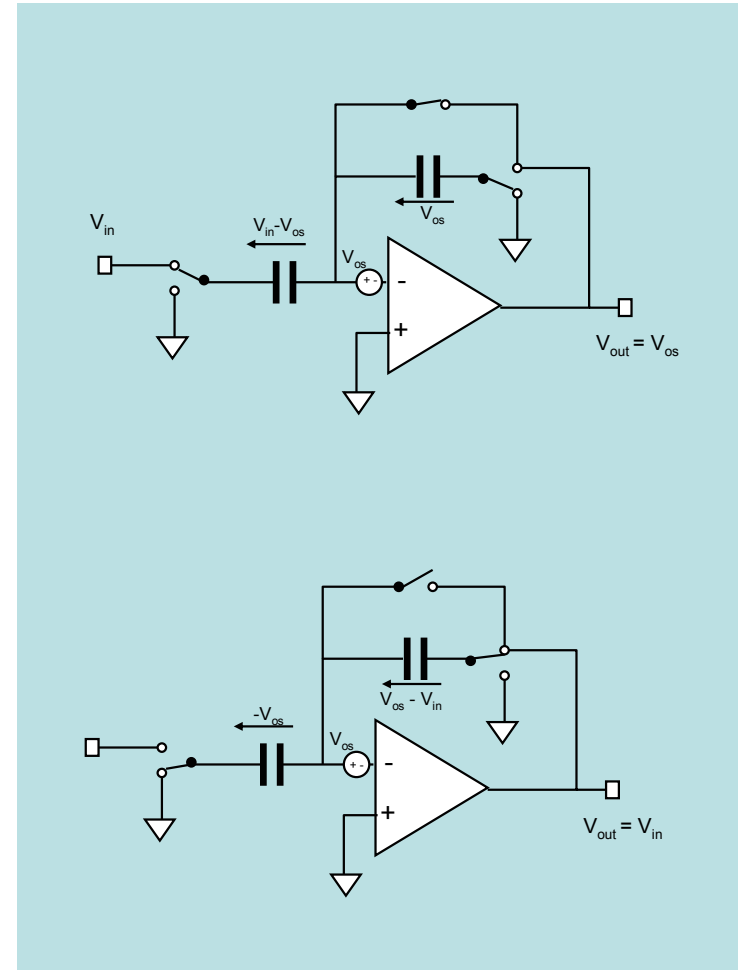- “Half-cycle” building blocks allow cancellation of offset voltage
 - GainHalf
 - GainHold
 - RectifierHalf
 - RectifierHold
 - SumDiff
- “Offset-compensated” in one clock phase only (return-to-zero or hold-with-offset in other phase)
- Gain-Bandwidth Product (GBP) and slew-rate are not infinite!
 - Selection of high-gain will limit max clock frequency (and vice versa) of RTZ CAMs



Achieving High-gain

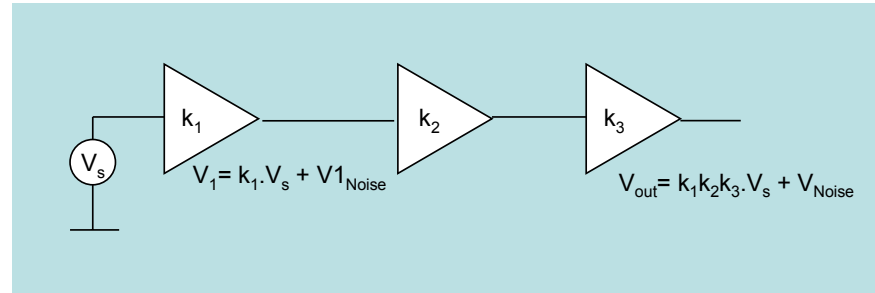- **Cascade stages – high-gain at front-end for low-noise**




$$V_{noise} = K \cdot \left(\frac{V_{1noise}}{k_1} + \frac{V_{2noise}}{k_1 k_2} + \frac{V_{3noise}}{k_1 k_2 k_3} \right)$$

- **Use offset-compensated CAMs when implementing large gains**
 - Remember GBP limitations – select appropriate clock frequency (but watch anti-aliasing requirements)



Phase Selection

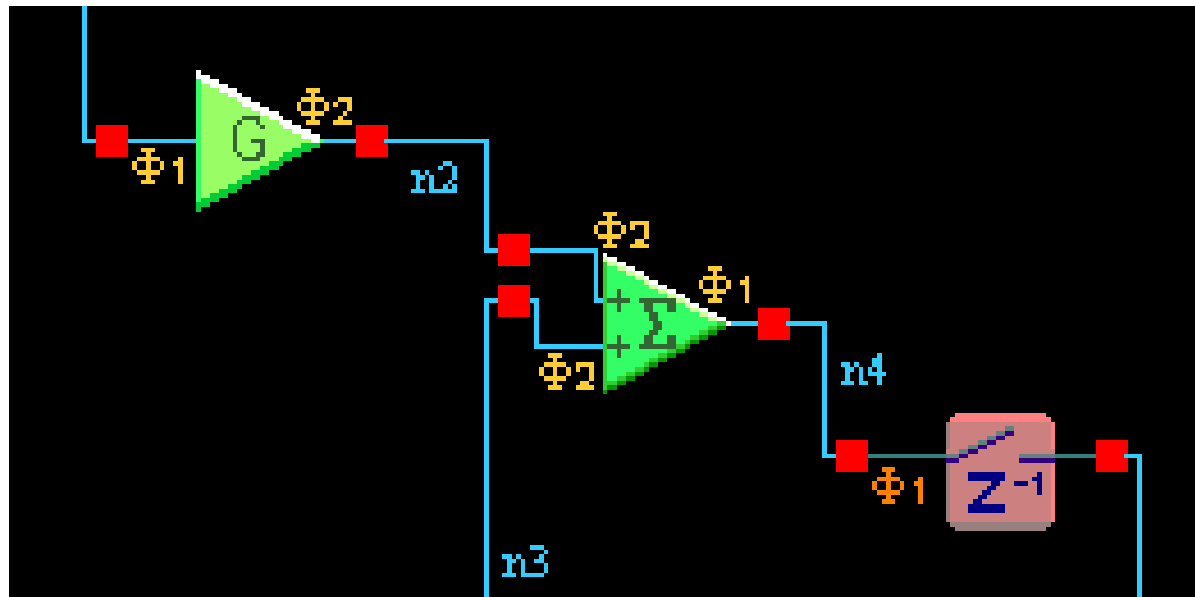- Some CAMs have outputs which are only valid (or offset-compensated) in one phase
- Make sure input-sampling and output-valid phases match!



Output Waveforms (1)

- Staircase outputs:

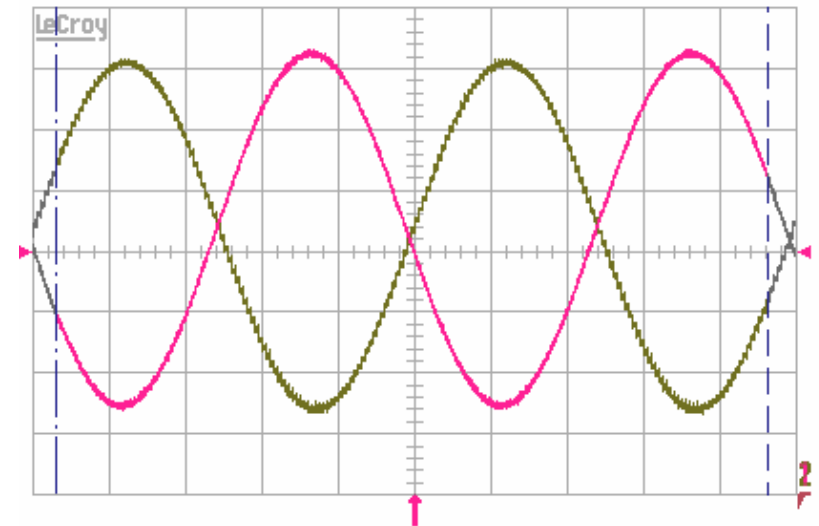
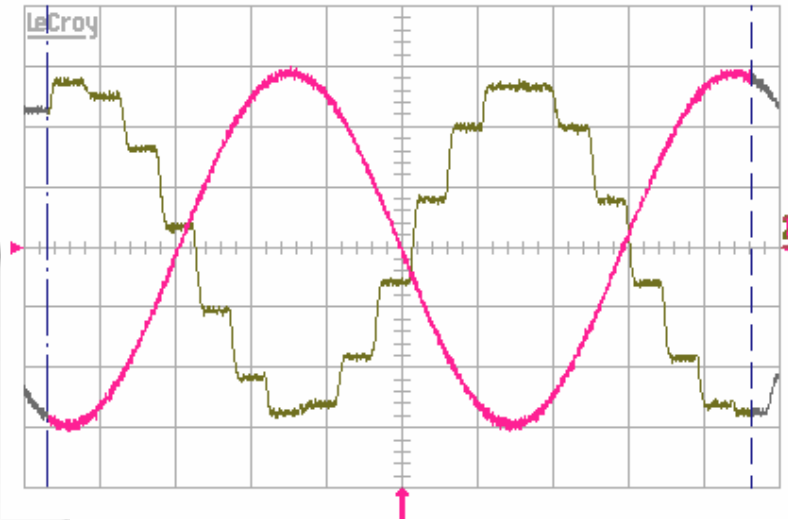


- Use high $f_{\text{clock}}/f_{\text{signal}}$ ratio to reduce step size and clock noise
- Keep $f_{\text{corner}}/f_{\text{signal}} > 30$ if using output cell filter
- If output is being sampled (eg by ADC), steps may be desirable !

Output Waveforms (2)


- **“Final-value” outputs**

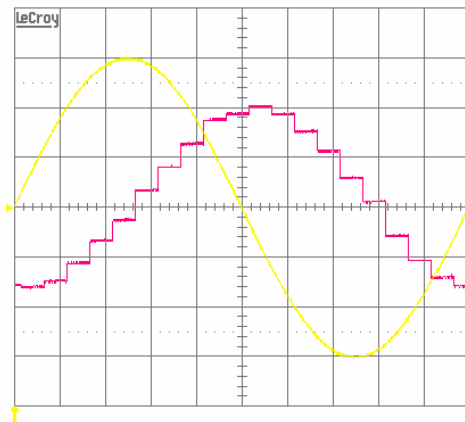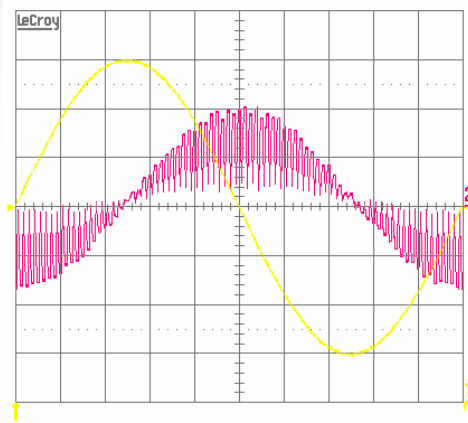- Differentiator (and transimpedance amplifier) outputs only reach their final value at the end of a clock phase
- Final-value CAM outputs need capturing by CAMs which sample in one-phase and produce a valid output in the next




- **Hold**
- **Non-inverting GainHalf**
- **Non-inverting SumDiff**
- **Non-inverting SumFilter**

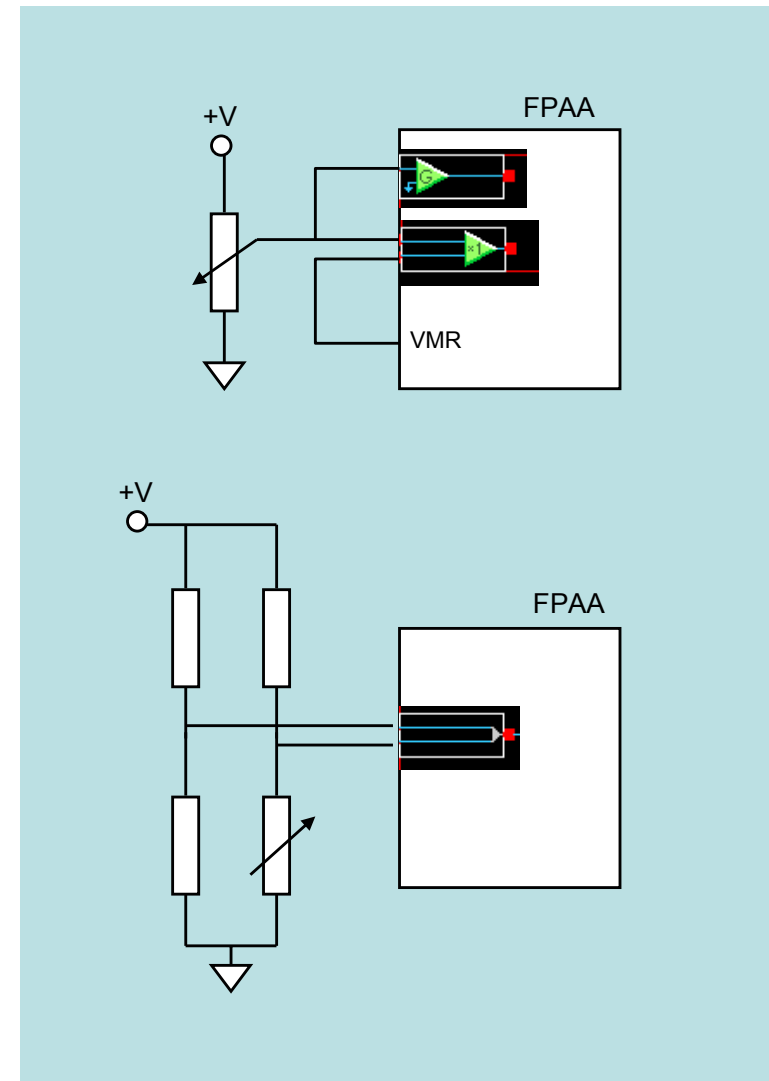- **Internal signal ground is 2 volts (VMR)**
 - Center inputs on 2V if possible (use Wheatstone bridge?)
 - Input range 0 – 4V
 - Convert external single-ended signals to internal differential signals for max dynamic range









Offset Removal

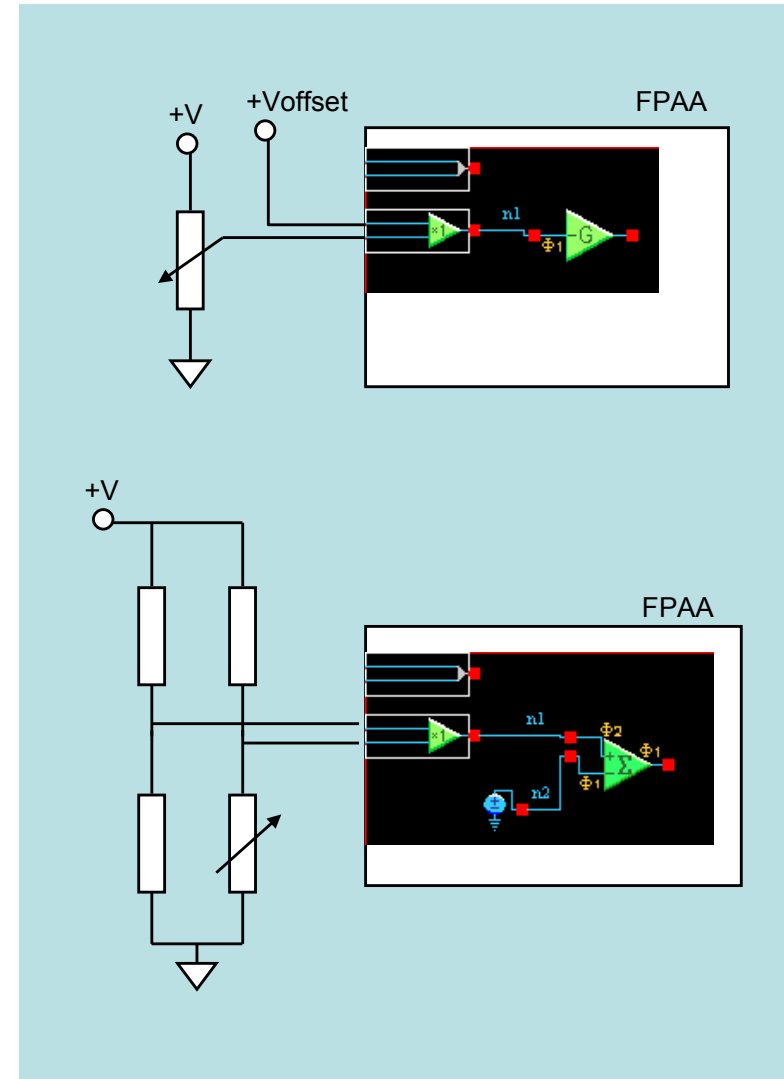- **Single-ended signals**
– apply offset to 2nd input pin
- **Differential signals** –
apply offset internally
- **Using differential signals gives better CM noise immunity**




Using the Chopper Input

- **“Chopping” modulates the input signal with a square wave**
 - Low freq noise and DC offsets are pushed out to the clock freq (for easy filtering)
- **Slewing and settling limitations mean the chopper output is not “ideal”**
 - To recover the “ideal” output, sample in phase2 *at twice the chopper frequency*
- **To boost the gain, use offset-compensated CAMs, *sampling in phase2 at twice the chopper frequency***

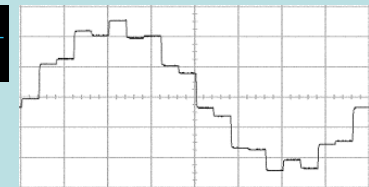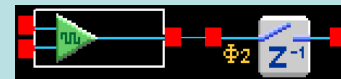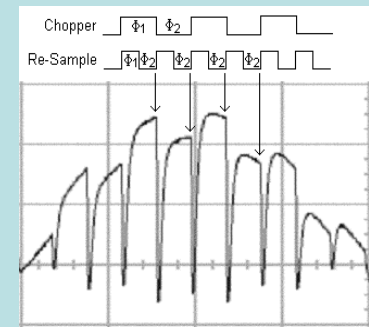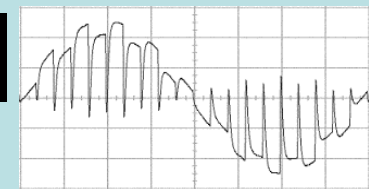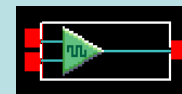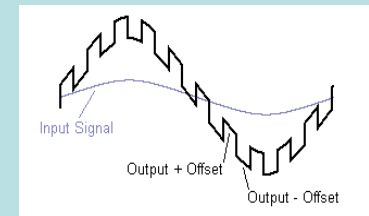


Noisy Environments

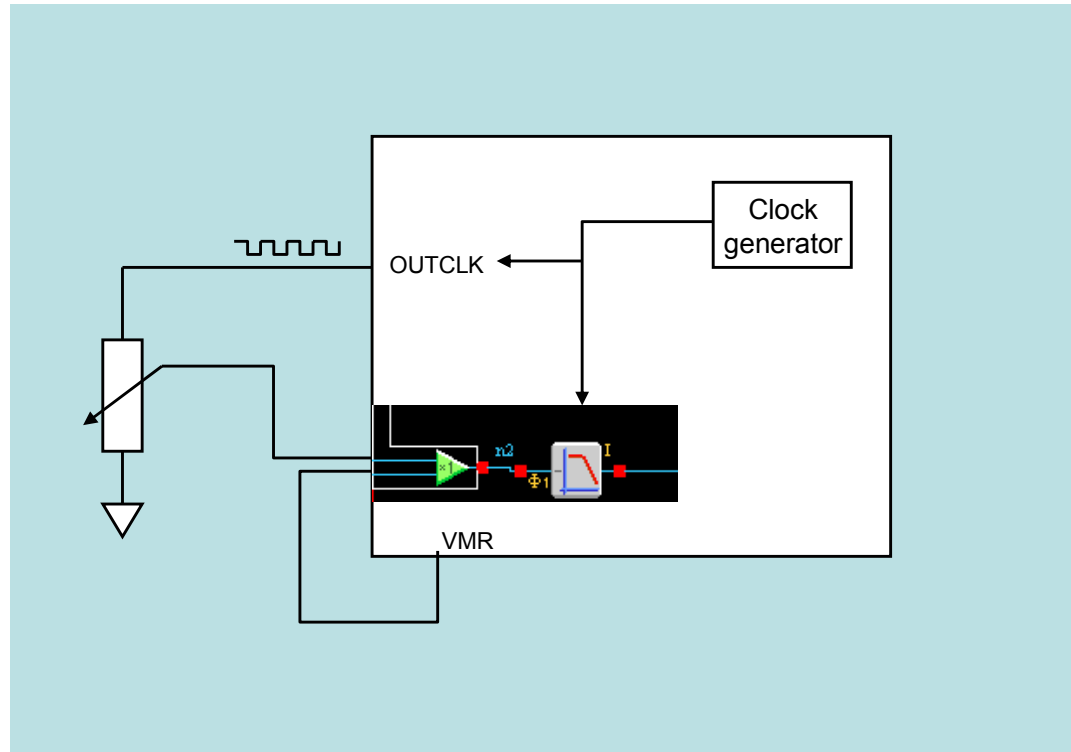- Use differential signals where noise can be made common-mode
- Use modulated sensor stimulus and synchronous demodulation (lock-in detection)



Phase Detection

- Synchronous demodulation



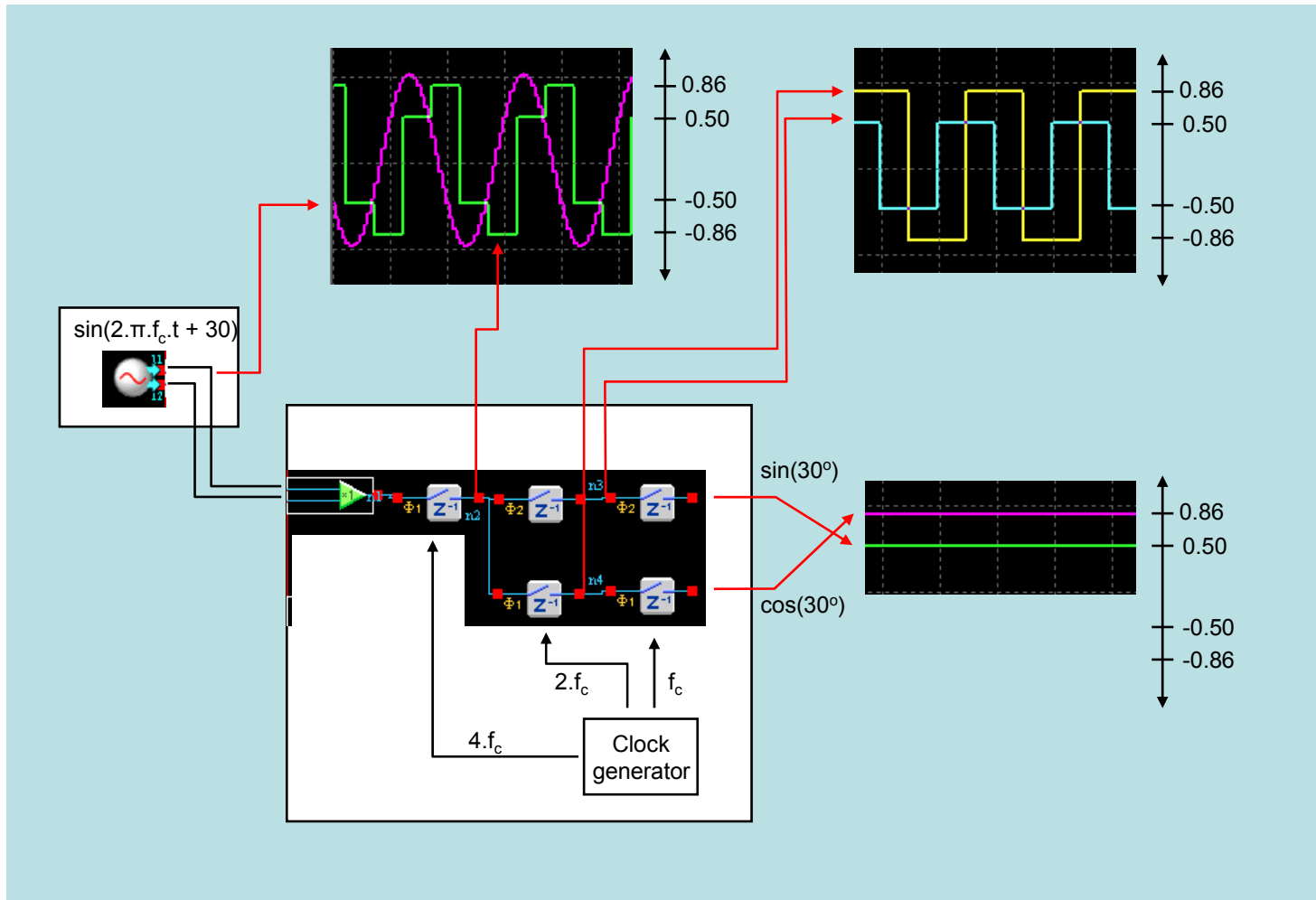


Anti-aliasing and Clock Selection

- **Input signal should be band-limited to $\ll f_{\text{clock}}/2$**
 - prevents hf noise adding to lf noise
 - Use a clock *at least* 5–10 times faster than the maximum signal
- **Use continuous-time not SC filtering**
 - attenuation at $f_{\text{clock}}/2$ should attenuate any hf signals by the required SNR
 - Keep $f_{\text{corner}}/f_{\text{signal}} > 30$ if using input cell filter
- **Lock-in detection averages out noise & signals except at harmonics of the modulation frequency**
 - Anti-aliasing not necessary (but will improve SNR if used)

Temperature-sensing (1)

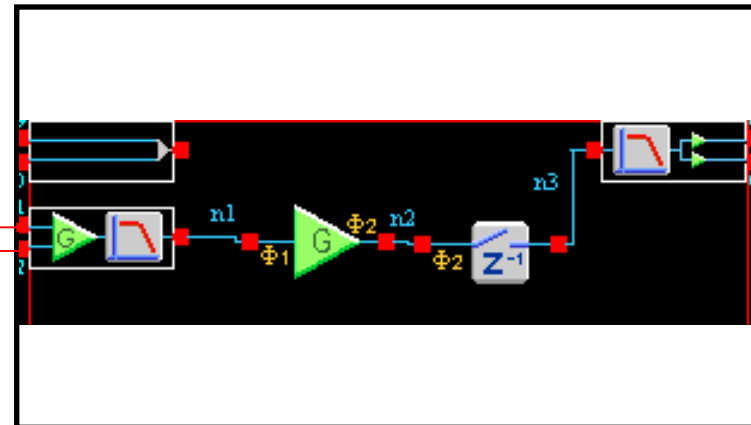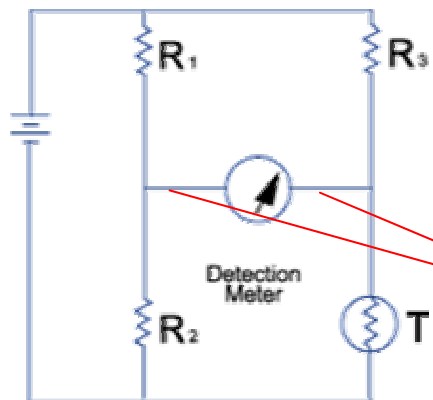
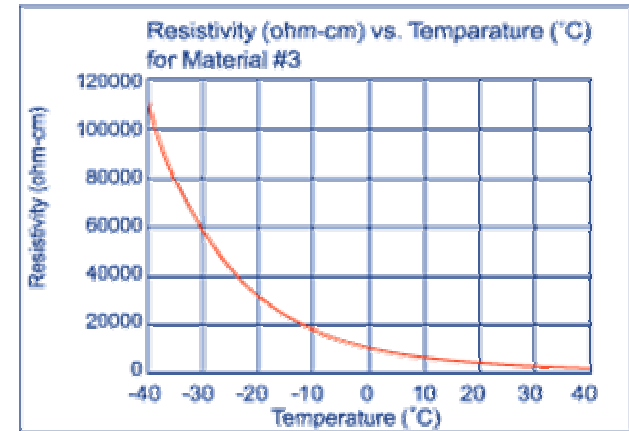
- Thermistors
 - Resistances range from 100 to 1Mohm
 - Typical current < 100uA to avoid self-heating



Temperature-sensing (2)

- **Thermocouples**

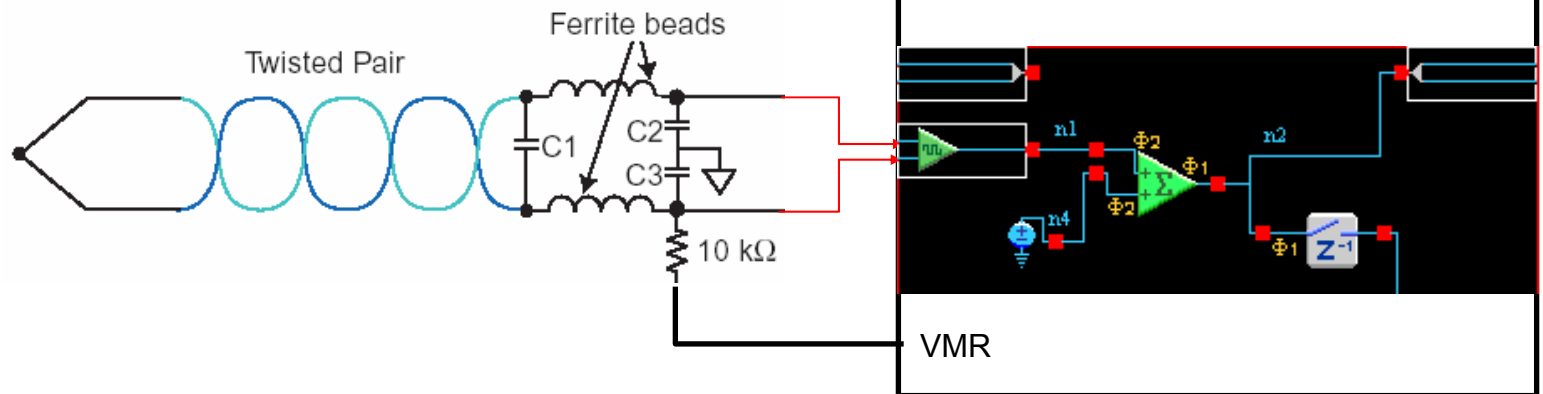
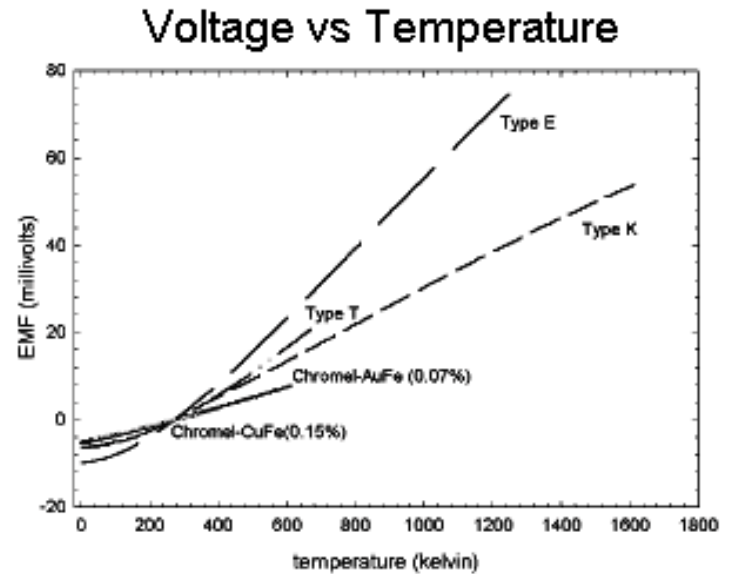
- Small voltage/degree C
- Prone to high levels of CM noise



Temperature-sensing (3)

- **Thermopiles**

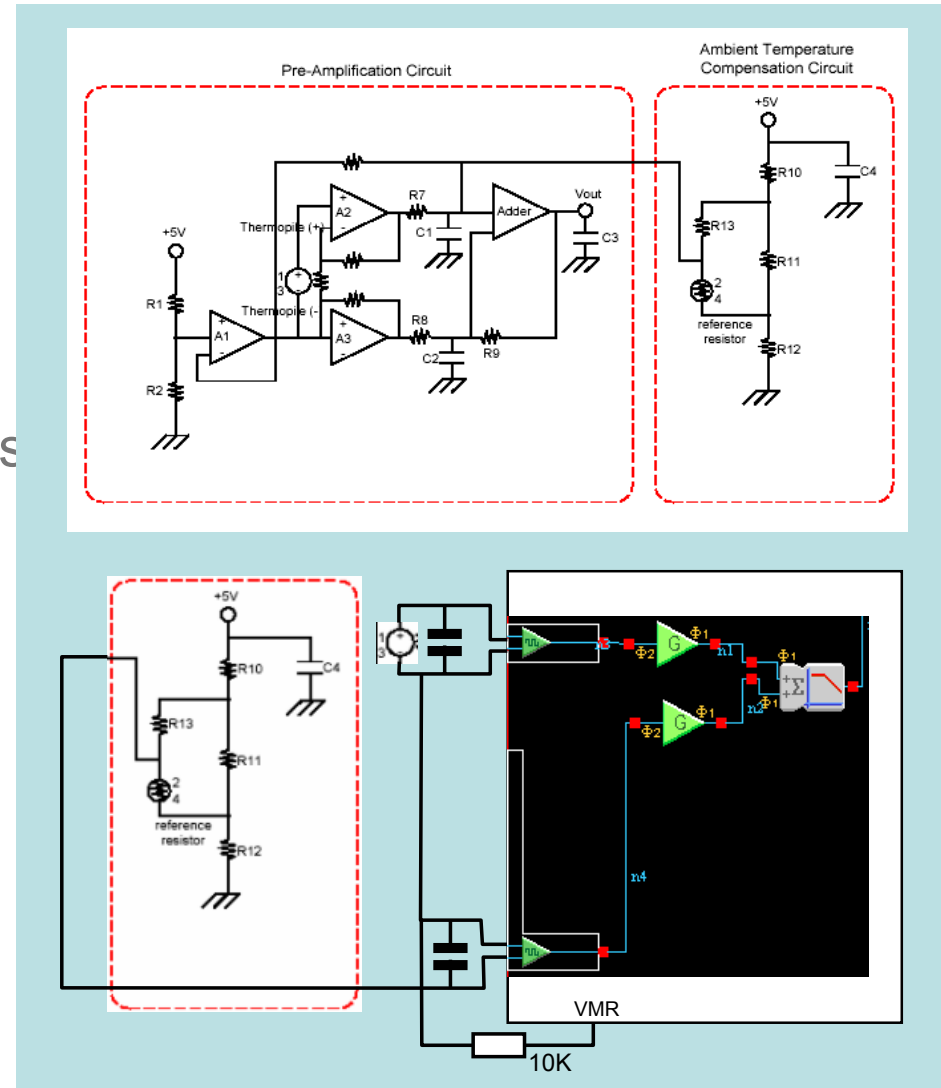
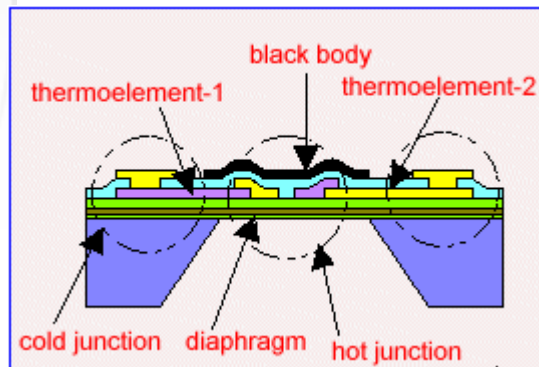
- Serially-interconnected thermocouples with “hot” and “cold” junctions
- “Hot” junction sensitive to received IR radiation
- Close proximity of junctions gives low sensitivity to ambient temperature



Position-sensing (1)

• Strain gauges

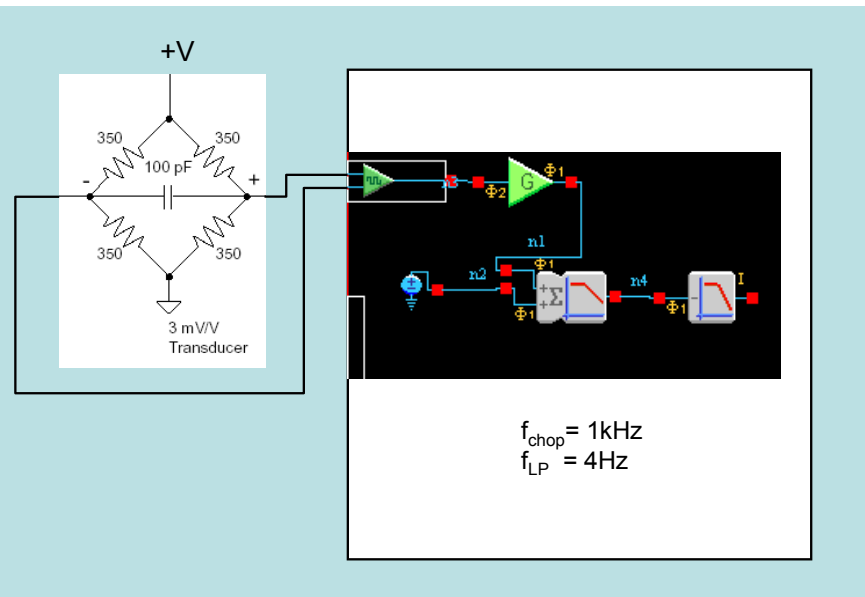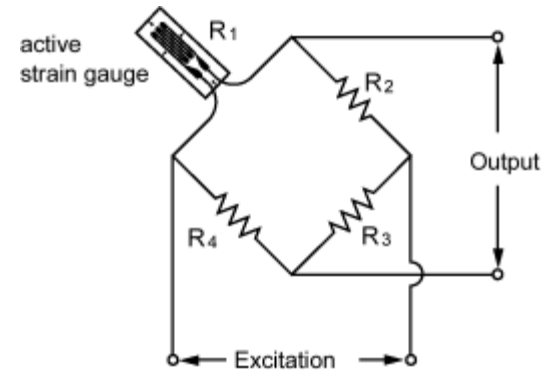- Typical output < 10 mV/V
- “Half bridge” has strain gauges in two arms:
 - doubles the output and compensates for thermal effects
- “Full bridge” has strain gauges in four arms:
 - re-doubles output and compensates for thermal effects



Position-sensing (2)



• LVDT

• Sensitivity ranges:

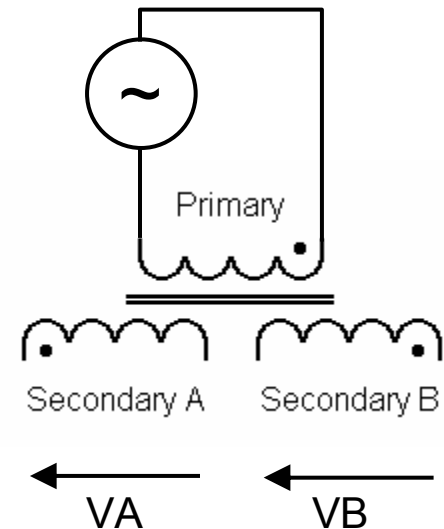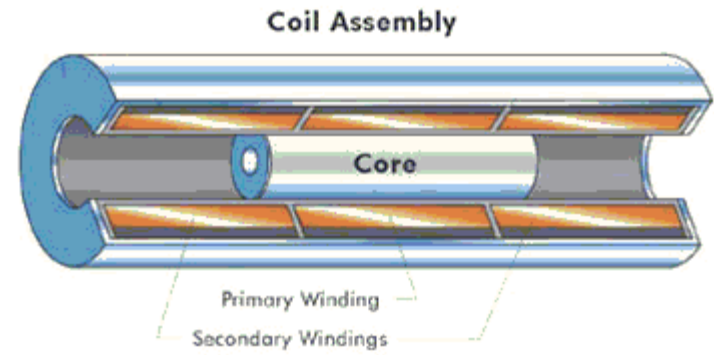
- 0.05 mV/V/0.001" for long stroke LVDTs
- 10 mV/V/0.001" for short stroke LVDTs

• Various signal processing techniques (eg):

- Rectify and filter AC signals, then:
 - Calculate $(V_A + V_B)/V_{\text{primary}}$ (insensitive to the amplitude of the driving signal, and gives some noise rejection).
 - Calculate the **ratio** of the difference and the sum of the secondary voltages i.e. $(V_A - V_B) / (V_A + V_B)$
- Measure the phase of the combined $V_A + V_B$ secondary voltage i.e. -180 degrees at one extreme, zero degrees at the null position, and +180 degrees at the other extreme.





LVDT-sensing

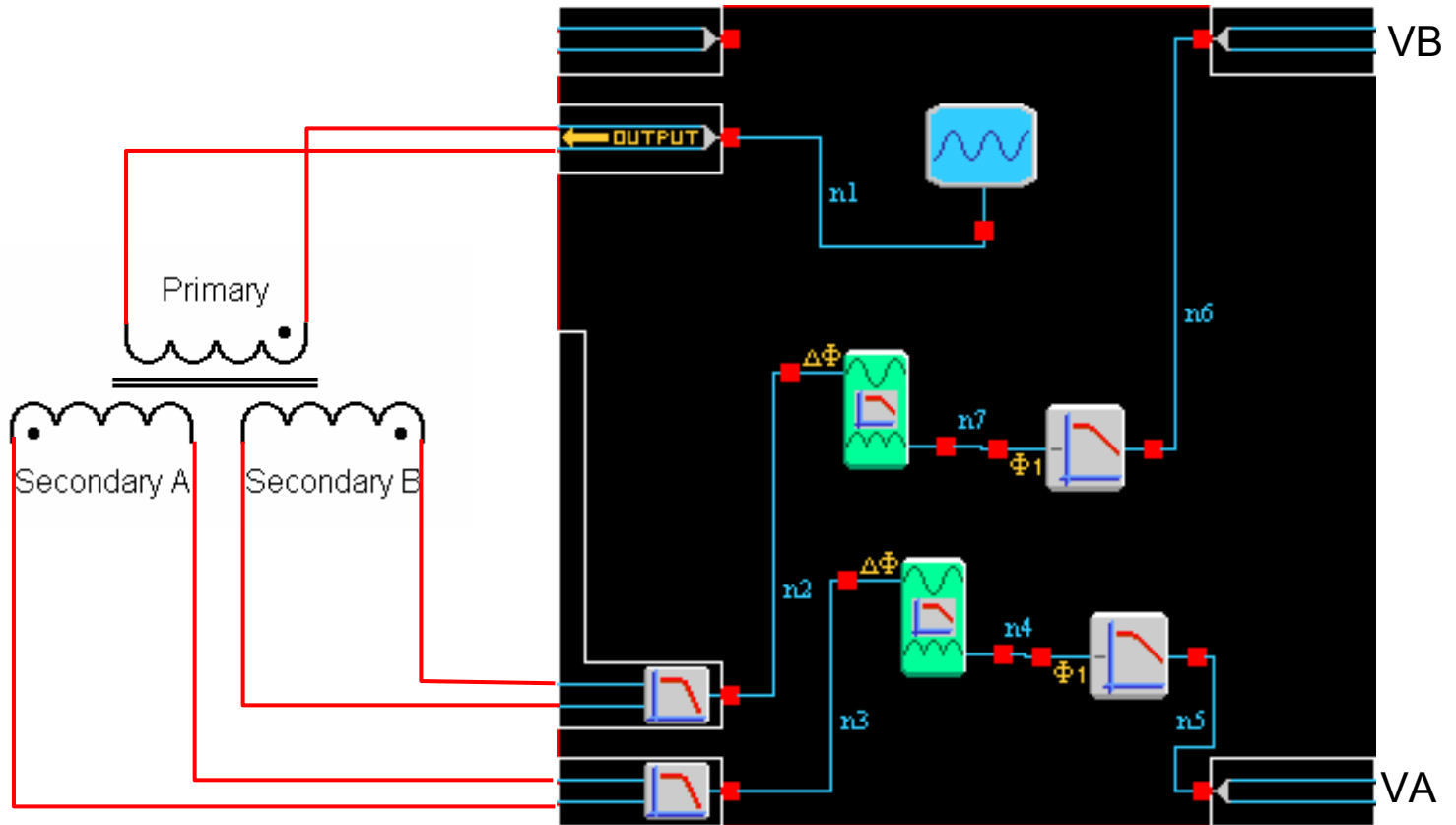

Magnetic-sensing


- **Hall effect devices**

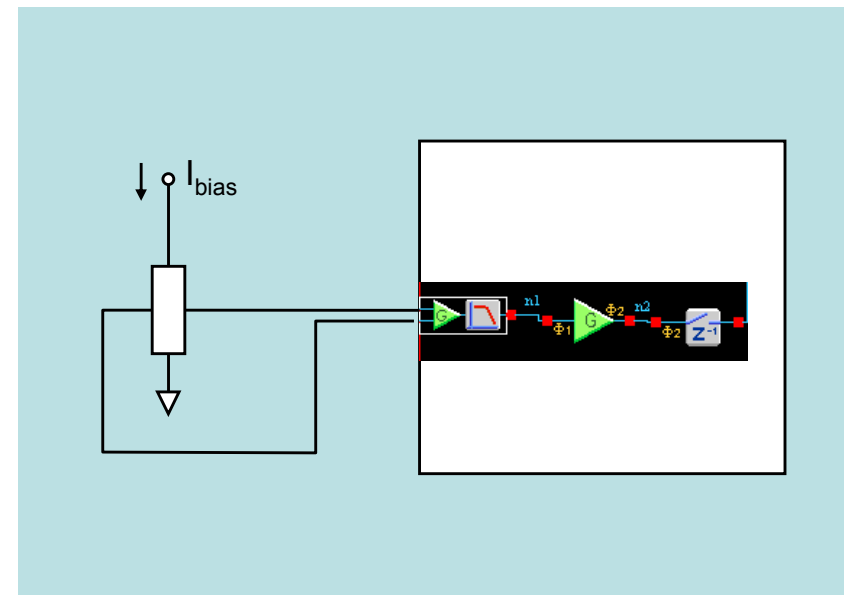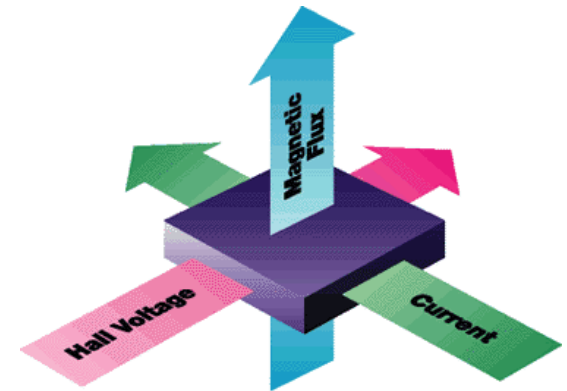- Usually driven with a **constant** current
- Differential output voltage, superimposed on a common-mode voltage approximately equal to half the excitation voltage.
- Typical sensitivity:
 - 1-100 mV/kG
 - (Refrigerator magnet: 200 gauss)
- Typical element resistance:
 - 1 to 10 ohms
- Typical excitation current:
 - 20 to 200 mA.
- Typical linearity:
 - 0.1% to 2%.




- **Photodiode/transistor**

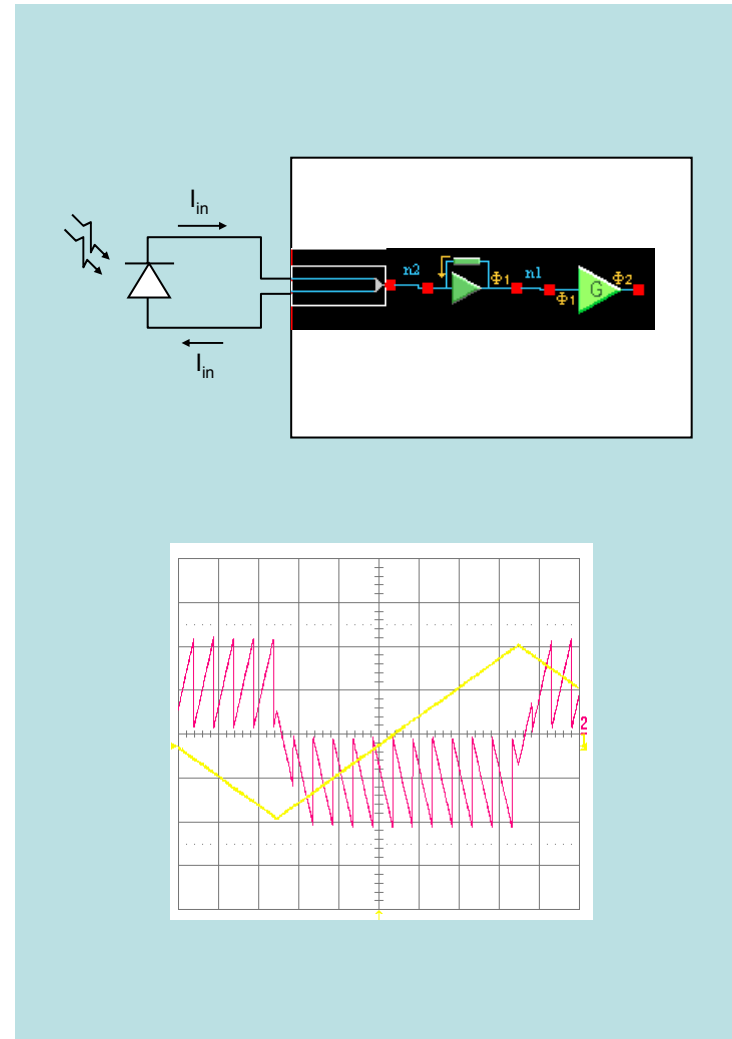- Photo-generated current develops a voltage across a feedback “resistor”
- Transimpedance is dependent on absolute capacitor values, **not** a capacitor ratio
- Transimpedance CAM output is only valid at the end of each clock phase – follow by an appropriate CAM



Sensor Linearization




NTC
thermistor-
based
sensor

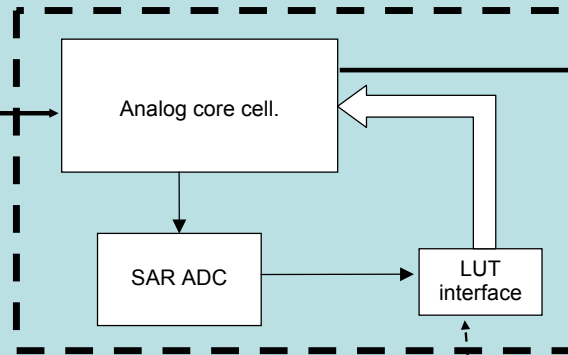

Sensor output is
non-linear

Signal dependent gain

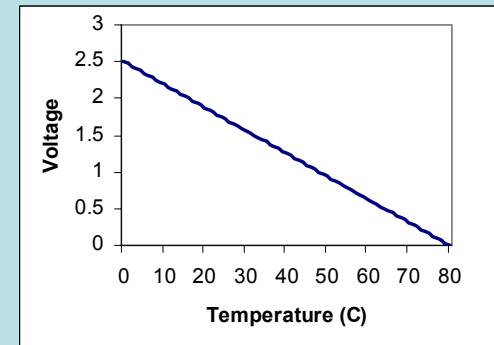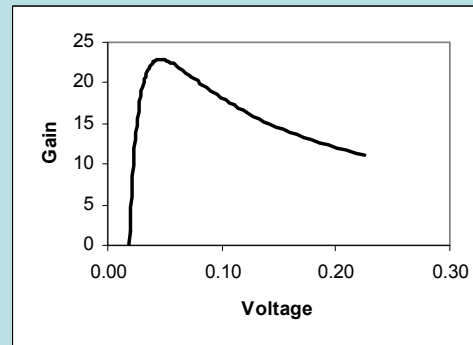
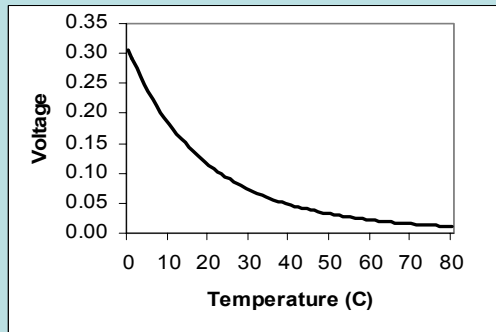
Linear
temperature/voltage
characteristic



Sensor Linearization


- **TransferFunction**
CAM

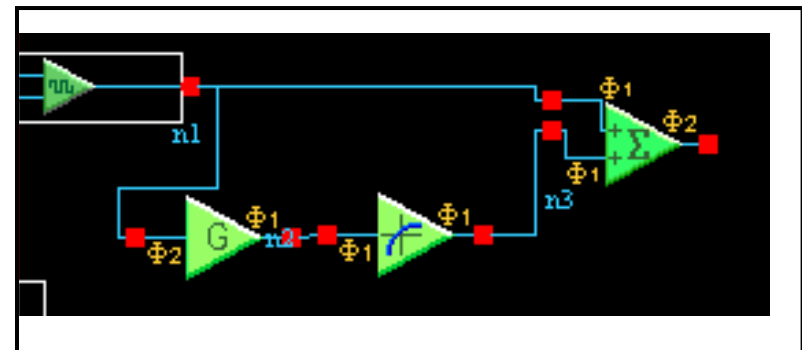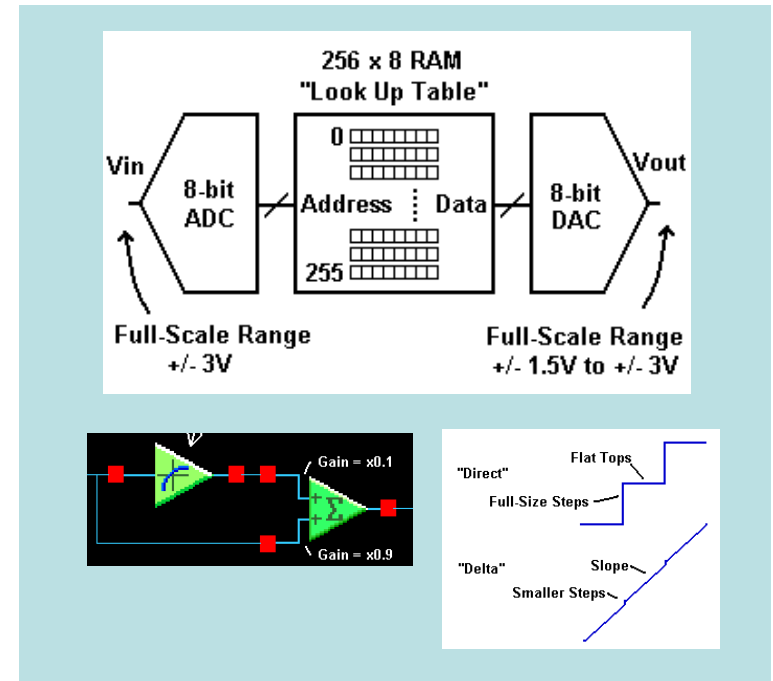- Quantizes gain – use full-scale input and output for minimum non-linearity
- When the input signal is nearly linear, use “delta” information rather than “direct”



Hardware Multiplexing

- State-driven dynamic reconfiguration:

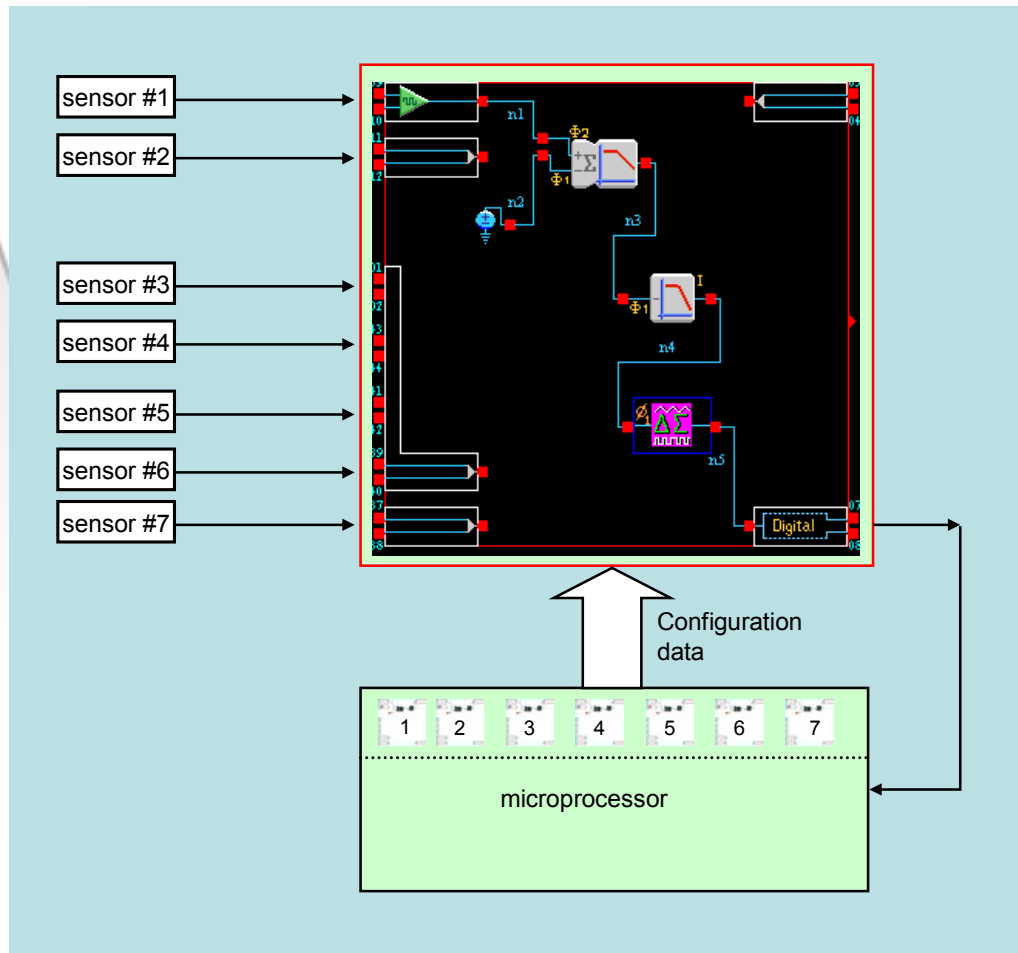

The screenshot shows the AnadigmDesigner2 software interface. The top window displays a circuit diagram with components labeled ID1:1, ID2:255, AN220EM4, and LOAD ORDER:1. Below the diagram is a C code snippet for state-driven dynamic reconfiguration:

```
void main()
{
    // Get the Primary Configuration data
    int dataSize = 0;
    const an_Byte* pData = an_GetPrimaryConfigData(an_chip1_Primary, &dataSize);

    // Send it
    Download(pData, dataSize, 1);

    an_Circuit nCircuit = an_circuit1_chip1_Data;
    while (1)
    {
        // Work out which circuit is needed next
        switch(nCircuit)
        {
            case an_circuit1_chip1_Data:
                nCircuit=an_circuit2_chip1_Data;
                break;
            case an_circuit2_chip1_Data:
                nCircuit=an_circuit3_chip1_Data;
                break;

            // etc., for the other cases

            default:
                nCircuit=an_circuit1_chip1_Data;
        }
    }

    // Get the transition data
    dataSize = 0;
    pData = an_GetCircuitTransitionData(nCircuit, &dataSize);

    // Send it
    Download(pData, dataSize, 0);

    // Pause while the measurement is taken

}
//end of main()
```